

Digital Design & Computer Arch.

Lab 8.1 Supplement: Full System Integration

Prof. Onur Mutlu

ETH Zürich

Spring 2024

6 May 2024

Lab 8 Overview

- You will build a whole single-cycle processor and write assembly code that runs on the FPGA board.
- Don't worry! You have 2 sessions for the lab, and it will give you up to 14 points (+6 points from the reports).
- You will learn how a processor is built.
- Learn how the processor communicates with the outside world.
- Implement the MIPS processor and demonstrate a simple "snake" program on the FPGA starter kit.

Lab 8 Sessions

- **Session I:** The Crawling Snake
- **Session II:** Speed Up the Snake

Lab 8 Session I: The MIPS Processor

- Download the Vivado project from the course website
- A lot of parts are **already implemented** for you!
- What you will have to implement:
 - ❑ Compute the **Instruction Memory** address and read the instruction.
 - ❑ Connect the **ALU**.
 - ❑ Compute the **Data Memory** address and add the necessary wires.
 - ❑ Instantiate the **Control Unit**.

Lab 8 Session I: Memory-Mapped I/O

- Your goal is to control the 7-segment display with your assembly program.
- You will need to **complete the I/O controller** so the output of the processor will be correctly mapped to the display.

I/O in Assembly


- How do we communicate with the display?
- Memory Mapped I/O
 - We designate specific addresses for the I/O
 - We can read and write to those addresses.
 - Example

```
# write contents of $t0 into memory at address 0x7FF0  
# so that the I/O controller can send it to the display
```

```
sw $t0, 0x7FF0($0)
```

Lab 8 Session I : The Crawling Snake

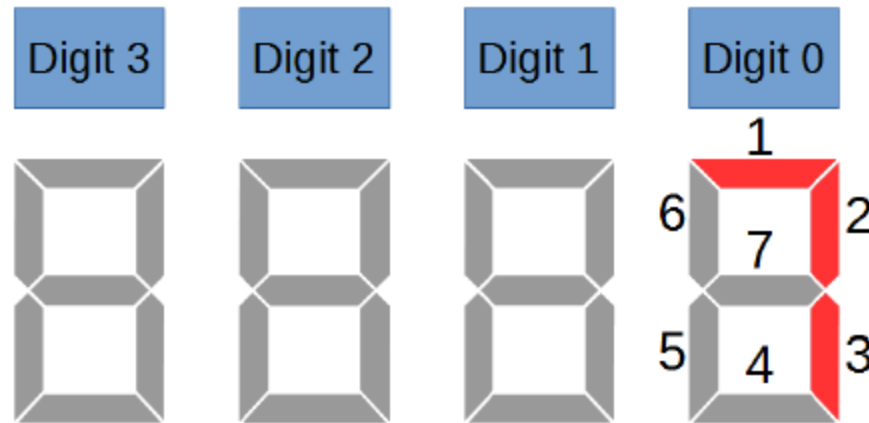- You learned how to **write assembly code** in Lab 7
- We provide you with the code for a **crawling snake** on the **7-segment display**



- We will run this program on the processor you build in this lab!

Lab 8 Session I : The Given Code

- Read the lab manual carefully! It contains important information that will save you a lot of time.
- The code contains `//TODO` markers to show you where you are supposed to add things.

Lab 8 Session I : The Given Code

- The lab manual tells you what files contain and which files you need to modify.

top.v	Top level hierarchy that connects the MIPS processor to the I/O on the FPGA board. <i>You will modify this file for Part 2.</i>
top.xdc	Constraints file of the top level. <i>You will modify this file for Part 2.</i>
MIPS.v	The main processor. <i>For Part 1, you have to add code inside of this file only.</i>
DataMemory.v (datamem_h.txt)	The initial content of the data memory (composed of 64 32-bit words). The datamem_h.txt file contains the data part of the assembly program in a hexadecimal form. This module "loads" the data. <i>You will only have to modify the .txt file if you do the challenges.</i>
InstructionMemory.v (insmem_h.txt)	The ROM (composed of 64 32-bit words) contains the program. The insmem_h.txt file contains the assembly instructions we want to run on the MIPS processor in a hexadecimal form. This module "loads" the instructions. <i>You will modify the .txt file for Part 2.</i>
RegisterFile.v	Register file that creates two instances of reg_half.v as read ports and has one write port. <i>This is the implementation of a register. You do not need to modify it.</i>
reg_half.v reg_half.ngc	Component describing a single port memory and binary description of how it is mapped in the FPGA. <i>These are used to implement the register. You do not need to modify it.</i>
ALU.v	ALU similar to the one from Lab 5. <i>You should not change anything in this file, but if you want, you can use your own implementation (just make sure that it works).</i>
ControlUnit.v	The unit that does the instruction decoding and generates nearly all the control signals. Table 7.5 on page 379 lists most of them and their truth tables (only the ALuOp signal is generated differently in the exercise). <i>This is just a combinational circuit, and it's already given; you don't need to change anything here.</i>
snake_patterns.asm	Assembly program corresponding to the datamem_h.txt and insmem_h.txt dump files that displays a crawling snake on the 7-segment display when all the parts are connected properly. <i>You have to modify this file for Part 2, where you will also learn how to generate the dump files.</i>

Lab 8 Session I : The Given Code

- For each `//TODO` in the code there is a part in the lab manual that explains what you are supposed to do.

```
// Memory Mapped I/O
assign IsIO = (ALUResult[31:4] == 28'h00007ff) ? 1 : 0; // 1: when datamemory address
// falls into I/O address range

// TODO Part 1
assign IsMemWrite = // Is 1 when there is a SW instruction on DataMem
address
assign IOWriteData = // This line is connected directly to WriteData
assign IOAddr = // The LSB 4 bits of the Address is assigned to IOAddr
assign IOWriteEn = // Is 1 when there is a SW instruction on IO address

assign ReadMemIO = IsIO ? IOReadData : ReadData; // Mux selects memory or I/O
// Select either the Data Memory (or IO) output or the ALU Result
assign Result = MementoReg ? ReadMemIO : ALUResult; // Slightly modified to include above
```

What's the difference between MemWrite, DataMemWrite, and IOWriteEn?			Signal		
			MemWrite	DataMemWrite	IOWriteEn
Instruction	SW instruction	on DataMem address	1	1	0
		on IO address		0	1
	Non-SW instruction	D.C. (don't care)	0	0	0

Lab 8 Session I : Verilog Endianness

- Verilog does not assume **endianness of buses**.
- The endianness is determined depending on **how you declare** the bus.
- `wire[10:0] A` is **little endian**.
- `wire[0:10] B` is **big endian**.

Lab 8 Session I : Verilog Endianness

- `wire[10:0] A` is **little endian**.
 - `A[10]` is the **most significant bit**
 - `A` ends in the least significant bit.
 - `[10], [9], ... , [0]`
- `wire[0:10] B` is **big endian**.
 - `B[10]` is the **least significant bit**
 - `B` ends in the most significant bit.
 - `[0], [1], ... , [10]`
- `A[1:0]` selects the lower 2 bits in both cases.

Last Words

- You will build a whole single-cycle processor and write assembly code that runs on the FPGA board.
- You will learn how a processor is built.
- Learn how the processor communicates with the outside world.
- Implement the MIPS processor and demonstrate a simple “snake” program on the FPGA starter kit.
- You will have some questions to answer in the report.

Report Deadline

23 May 2025 23:59

Digital Design & Computer Arch.

Lab 8.1 Supplement: Full System Integration

Prof. Onur Mutlu

ETH Zürich

Spring 2024

6 May 2024